


Low Cost PV Regulator



Homebrew

Tom Kirkgaard

©1999 Tom Kirkgaard

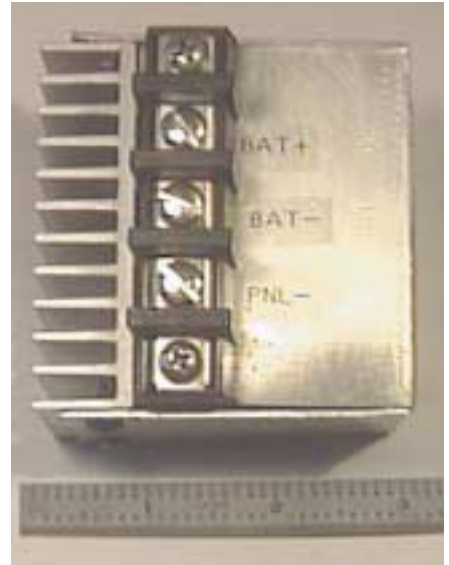

Building solar panels or batteries is beyond the capabilities of the average person. Building a regulator for your PV system is not.

This regulator design is capable of handling up to 30 amps for a 12 volt or 24 volt system. To build it, you need to be able to read schematics and know basic construction techniques. If you've built small homebrew projects before, this should be no problem.

A regulator's job is to connect the solar panels to the battery when it needs charging, and to disconnect them when it doesn't. The regulator should also prevent battery power from being dissipated in the solar panels after the sun has gone down. The ideal regulator would not generate any heat while controlling your precious solar power. This regulator design achieves this with a minimal number of parts, at low cost.

Operation

The regulator connects or disconnects the panel dependent on the battery voltage. The user sets this voltage, so any type of battery can be accommodated. The switching portion of the regulator uses a field effect transistor, or FET (Q2). FETs are amazingly efficient. At 20 amps, I measured only 0.2 volts drop across the FET used in this regulator.

The brain of the regulator is a 555 IC. This part is usually used as an oscillator, but it contains the circuitry needed for an on/off regulator. Pin 5 in U1 sets the reference voltage for U1. The output of U1 pin 3 goes to 12 volts when the input to U1 pin 2 falls below one half of pin 5. The output of U1 pin 3 goes to 0 volts when the input to U1 pin 6 rises above pin 5.

The battery voltage is divided by potentiometers R2 and R3 and applied to U1 pins 6 and 2. Setting the on/off voltage limits with R2 and R3 allows a voltage range. Within this window of voltage, the regulator can be on or off depending on whether the battery voltage is rising or falling. Below the lower limit, the regulator is always

on. Above the upper limit, the regulator is always off. In operation, when the regulator is on, the battery voltage rises to the upper limit, then shuts off. It will remain off until the battery voltage drops below the lower limit, then the regulator turns on.

Preventing discharge at night is easily accomplished with a diode. But unless you pick your diode carefully, it can be a source of power loss. Diodes have a small voltage drop in the forward direction. A standard power diode can have a drop of 0.6–1 volt. At 15 amps, this would translate into 9–15 watts of wasted power. In this project, we use a Schottky diode, which can reduce the voltage drop to 0.4–0.7 volts. At 15 amps, it wastes 6–10.5 watts of power. This may seem fussy, but you probably paid \$5 a watt when you bought the panels.

Construction

There are 12 and 24 volt versions of this regulator. For the 12 V version, install all the J1 jumpers (denoted by connecting the two dots to the left and right of the J1 designator) and install all parts *except* the ones beginning with (2). For the 24 V version, install all the J2 jumpers and install all parts *except* the ones beginning with (1).

A good approach would be to install all the parts except D1 and Q2 on a perfboard. Layout isn't critical, but it would be wise to allow for a good common for all parts going to ground. When building, keep in mind that the regulator will most likely be connected to a large battery. Make sure there is no possibility of a short. A small aluminum box can serve as a protective enclosure and heat sink.

My prototype had a barrier terminal block with three screw terminals on the top and solder tabs on the bottom. This was used to make the solar panel and

in the wiring from the regulator to the battery. If this occurs, increase the *on* to *off* voltage span and use larger wire from the regulator to the battery. See examples of systems in other *Home Power* articles for safe installation of regulators.



Above: The FET installed.

Parts List

Qty	Code	Description	Cost
1	Q1	2N3906 PNP transistor	
1	Q2	IRFP048 N channel HEXFET	
1	VR1	1N754 6.8 V 0.5W zener diode (1)	
3	C1-5	1μF 25 V electrolytic capacitors (1)	
5	C1-5	1μF 25 V electrolytic capacitors (2)	
2	R1,4	3.3K 0.25W 5%	
2	R2,3	20K ten-turn trimmer potentiometer	
1	R5	100K 0.25W 5%	
1	R6	470K 0.25W 5%	
1	R7	6.8K 0.25W 5% (2)	
1	D1	30CPQ060 30 amp Schottky diode	
1	U1	LM 555 timing circuit	
1		8 pin DIP IC socket	
1	U2	LM7805C or LM340T-15 15 V reg. (2)	

Total

Lead Assignments

	Q2	D1	U2
	1 Gate	1 Anode	1 Input
	2 Drain	2 Cathode	2 Common
	3 Source	3 Anode	3 Output
Tab	Tab Drain	Tab Cathode	Tab Common

Q2, D1, and U2 have similar style cases

Access

Author: Tom Kirkgaard, 154 N. Berkeley Ave., Pasadena, CA 91107 • 310-662-7528 takirkgaard@mail.hac.com

Sources for parts:

Radio Shack, 100 Throckmorton St., Fort Worth, TX 76102 • 800-843-7422 • 817-415-3011
 Fax: 817-415-3240 • support@tandy.com
 www.radioshack.com

Digi-Key, PO Box 677, Thief River Falls, MN 56701-0677 • 800-DIGIKEY • 218-681-6674
 Fax: 218-681-3380 • sales@digikey.com
 www.digikey.com

International Rectifier, 233 Kansas St., El Segundo, CA 90245 • 310-252-7105 • Fax: 310-252-7903
 procntr@irf.com • www.irf.com



Y2K RESOURCES

Catalog of TOOLS • Water Storage • Fuel Storage • Y2K Shopping Lists • Resources, How-to Plans and Simple, Low-Cost Ideas!

<http://lowcostliving.com>

New England

S O L A R H O M E S TM

Solar Farmhouse TM

Standard Features
of a New England Solar Home

- Generous unobstructed south-facing roof area
- Passive solar configuration w/ dedicated sunspace
- Open light-filled interiors
- Standard & Custom Plans can be quoted for shipments of stress skin panel or pre-fab homes

Contemporary sunlit homes that you can build today!

For our free brochure contact us at:

New England Solar Homes
 18 Porter Street
 Somerville, MA 02143
tel 617 628 0852 **fax** 617 628 9545
email nesh@ecobuild.com **web** www.ecobuild.com

Plan Set Options:

- 1 Standard Plans
- 2 Std. Plans Customized
- 3 Full Custom

Call or write for price list.